

Design Notes Expt 5

Setting the differential input resistance

$$R_{id} = 2r_{be} = \frac{2\beta_o}{g_m} = \frac{2\beta_o}{40I_C}$$

So bias current, I_O in differential amplifier is

$$I_O = 2I_C = 2 \frac{2\beta_o}{40R_{id}}$$

$$I_O = \frac{\beta_o}{10R_{id}}$$

Now to design the Widlar current mirror to bias the diff amp stage.

$$R_E I_O = V_T \ln\left(\frac{I_{ref}}{I_O}\right) \text{ or } I_{ref} = I_O \exp\left(\frac{I_O R_E}{V_T}\right)$$

Don't know R_E or I_{ref}

$$\text{Try } I_O R_E = V_T$$

$$\text{Then } I_{ref} = I_O \exp(1)$$

OR Set $I_{ref} = 10 \times I_O$ then

$$R_E = \frac{V_T}{I_O} \ln(10)$$

Resistor in other branch of CM is

$$R = \frac{V_{CC} + V_{EE} - 0.6}{I_{ref}}$$

Gains

Gain of differential amplifier

$$A_{Vd} = \frac{1}{V_T} \frac{V_{An} V_{Ap}}{V_{An} + V_{Ap}}$$

Gain of CE stage (assume CC gain is unity)

$$A_{VT} \approx A_{Vd} \times A_{VCE}$$

$$\text{So } A_{VCE} > \frac{5 \times 10^5}{A_{Vd}}$$

$$A_{VCE} = \frac{1}{V_T} \frac{V_{An} V_{Ap}}{V_{An} + V_{Ap}}$$

Calculation for input resistance of CC coupling stage

$$R_i(CC) = r_{be}(CC) + (1 + \beta_o)R_E // R_L$$

$$R_E // R_L = \frac{R_E r_{be}(CE)}{R_E + r_{be}(CE)}$$

Set $R_i(CC)$ to be much bigger than the output resistance of the Diff/ amp stage (which acts as the source resistance of the CC stage):

$$R_o^{DA} = \frac{\frac{V_{An}}{I_C} \times \frac{V_{Ap}}{I_C}}{\frac{V_{An}}{I_C} + \frac{V_{Ap}}{I_C}}$$

(need to try a bias current for the common emitter, CE stage)

Then get a quadratic equation for the CC bias current. Use this to calculate the gain of the CC stage

$$A_v = \frac{g_m R_E // R_L}{1 + g_m R_E // R_L} = \frac{g_m R_E // r_{be}(CE)}{1 + g_m R_E // r_{be}(CE)}$$

Output resistance of op-amp (set by another CC stage)

$$R_o = \frac{r_{be} + R_S}{1 + \beta_o} // R_E, \quad R_o = \left(\frac{r_{be}}{\beta_o} + \frac{R_S}{\beta_o} \right) // R_E \quad \text{This } r_{be} \text{ is that of CC} \quad (\beta_o = g_m r_{be})$$

$$R_o = \left(\frac{r_{be}}{\beta_o} + \frac{R_S}{\beta_o} \right) // \frac{V_{EE}}{I_C}$$

The source resistance, R_S is the output resistance of the previous stage (CE) – see equation for the differential amplifier.

Set R_o to meet the specification; rearranging gives a quadratic equation for this CC bias current.